



Lecture 14

-- Laplace Transform in Circuit Analysis



V-I relations of R,L,C

• R
$$U_R(s) = RI_R(s)$$

• C
$$V(s) = \frac{1}{sC}I(s) + \frac{V_0}{s}$$

$$I(s) = sCV(s) - CV_0$$


• L
$$I(s) = \frac{1}{sL}V(s) + \frac{I_0}{s}$$

$$V(s) = sLI(s) - LI_0$$



S-domain circuit models for a capacitor


s-Domain Circuit Models

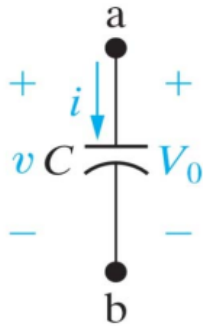


$$i(t) = C \frac{dv(t)}{dt}$$

For a capacitor
(with initial conditions)

$$I(s) = sCV(s) - CV_0$$

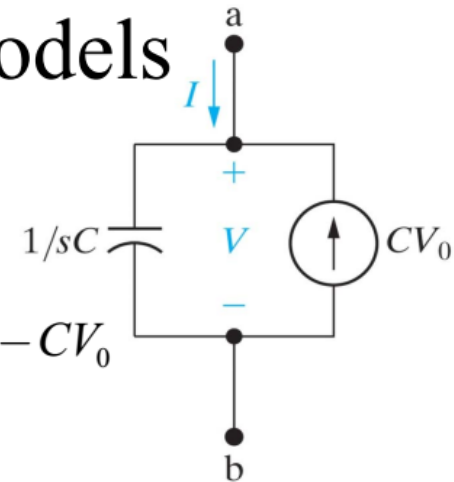

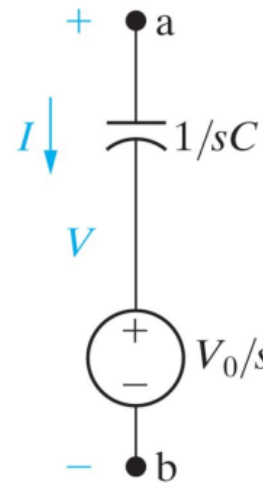
$$V(s) = \frac{1}{sC} I(s) + \frac{V_0}{s}$$



S-domain circuit models for an inductor

s-Domain Circuit Models

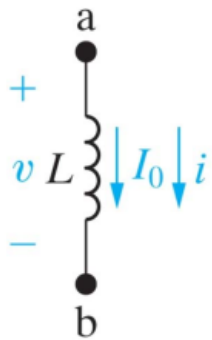


$$v(t) = L \frac{di(t)}{dt}$$


For an inductor
(with initial conditions)



$$V(s) = sLI(s) - LI_0$$

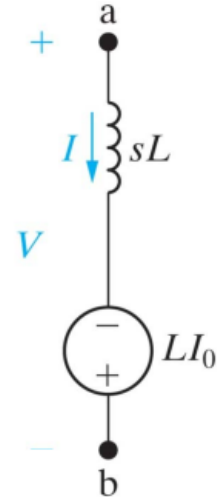








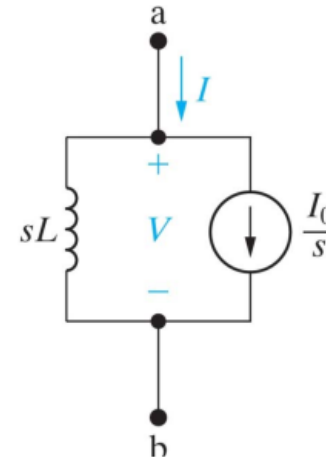
$$I(s) = \frac{1}{sL} V(s) + \frac{I_0}{s}$$





Time domain

s-domain

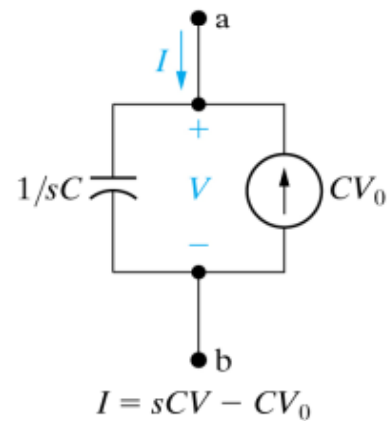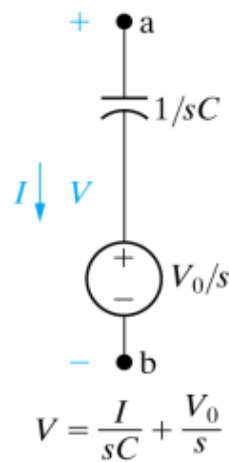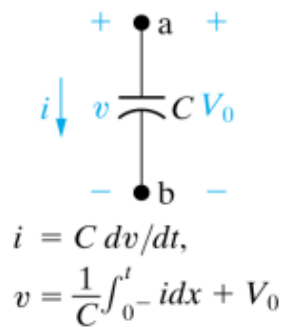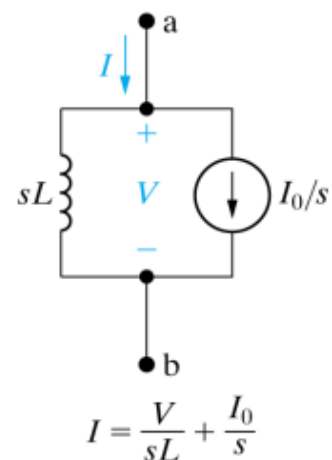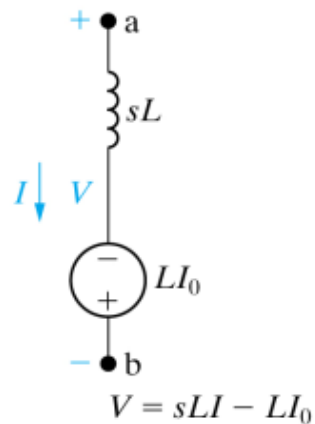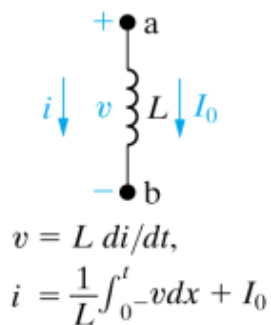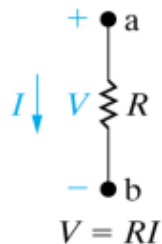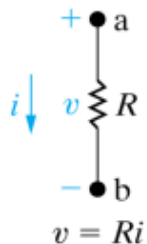



D.C. sources and Dependent Sources

- The models for dependent sources are easy to develop, drawing from the simple fact that if the Laplace transform of $f(t)$ is $F(s)$, then the Laplace transform of $af(t)$ is $aF(s)$ — the linearity property.

$$\mathcal{L}[av(t)] = aV(s)$$

$$\mathcal{L}[ai(t)] = aI(s)$$




Steps in Applying the Laplace transform

- **Transform the circuit from the time domain to the Laplace (s) domain, including initial conditions.**
--The elegance of using the Laplace transform in circuit analysis lies in (1) transforming the differential equation into an *algebraic* equation; and (2) automatic inclusion of initial conditions in the transformation process, thus providing a complete (**transient and steady-state**) solution.
- **Solve the circuit using nodal analysis, mesh analysis, source transformation, superposition, or any other analysis technique with which we are familiar.**
- Take the inverse transform of the solution and thus obtain the solution in the time domain.



Example 1

Assuming no initial energy storage, find $i_1(t)$ and $i_2(t)$ for $t > 0$.

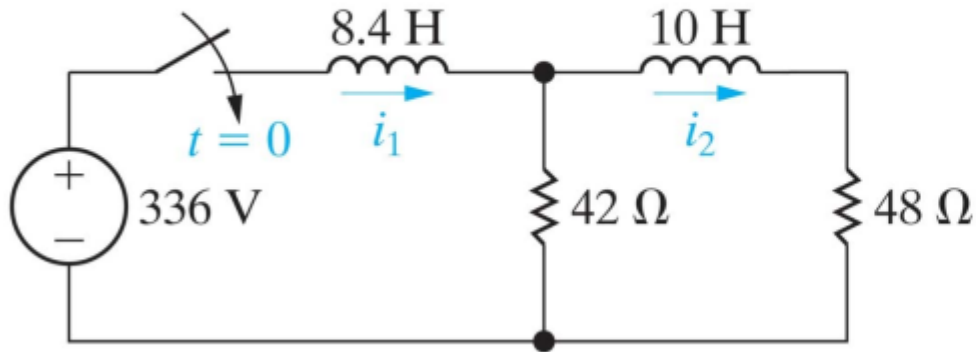






Example 2

Given $V_c(t=0) = 2\text{V}$, determine $v_o(t)$ for $t > 0$

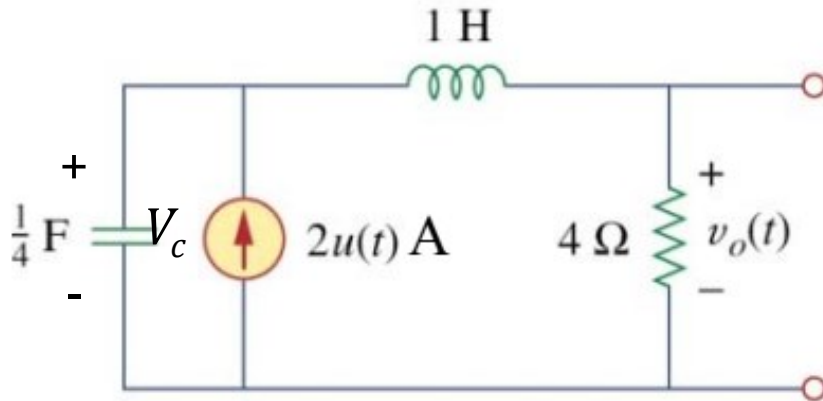




Example 3

- Find (1) the voltage across the capacitor
(2) current through the inductor



assuming that $v_s(t) = 10u(t)$ V, and given that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.

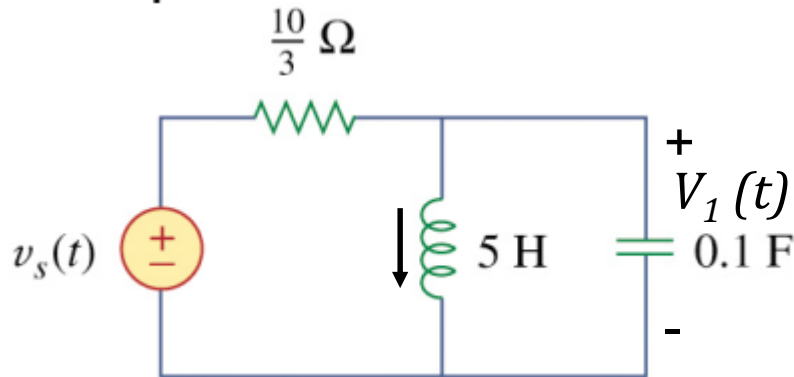

Example 3

- Find (1) the voltage across the capacitor
(2) current through the inductor

assuming that $v_s(t) = 10u(t)$ V, and assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor.

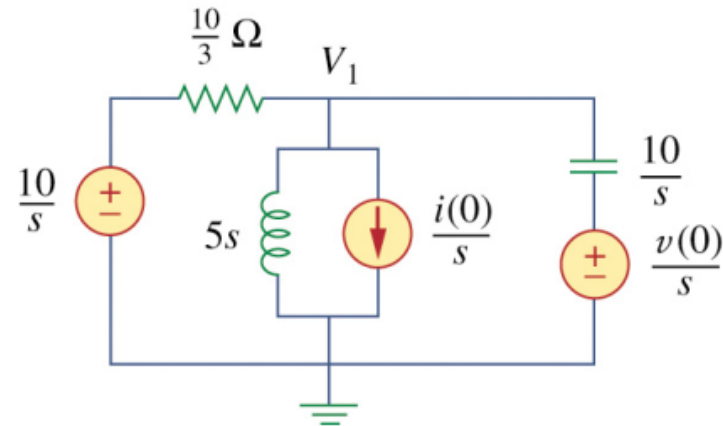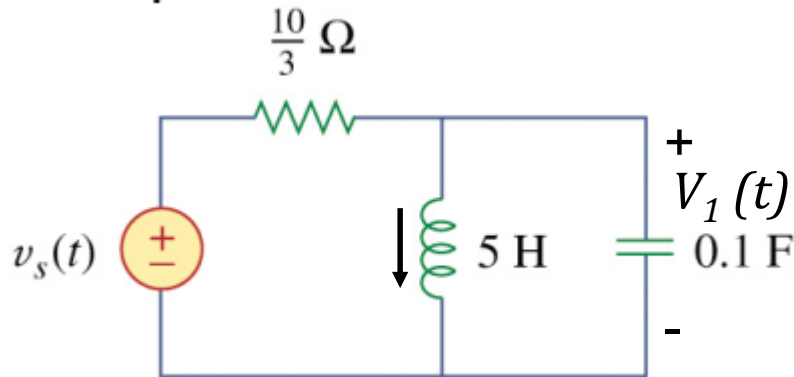








Example 4

- Find $v_o(t)$ for $t > 0$

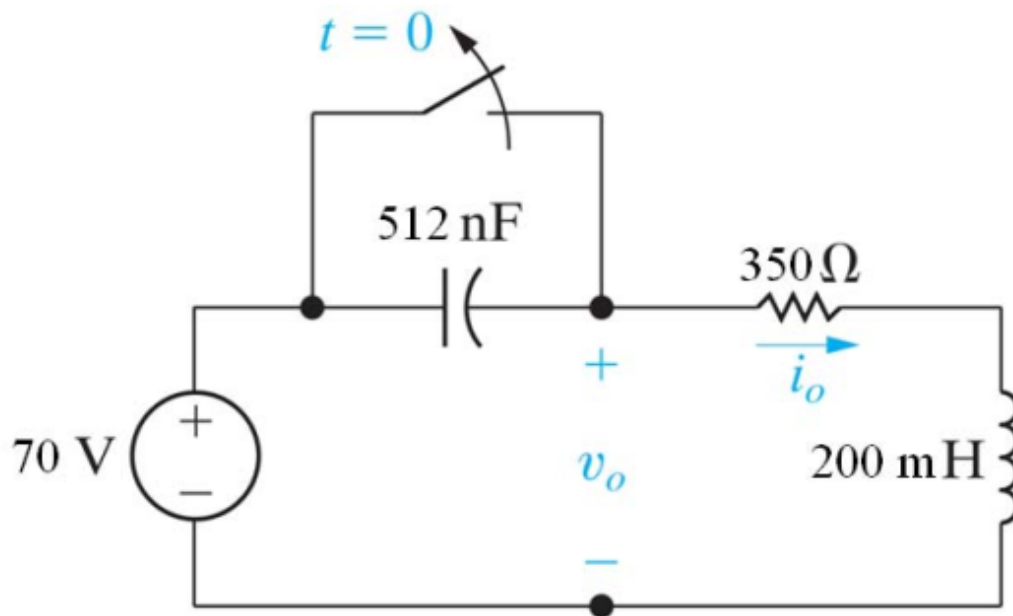





$$V_0(s) = \frac{70s - 268,125}{s^2 + 1750s + 9,765,625} = \frac{K_1}{(s + 875 - j3000)} + \frac{K_2}{(s + 875 + j3000)}$$

$$K_1 = \left. \frac{70s - 268,125}{(s + 875 + j3000)} \right|_{s=-875+j3000} = \frac{70(-875 + j3000) - 268,125}{[(-875 + j3000) + 875 + j3000]} = 65.1 \angle 57.48^\circ$$


$$K_2 = \left. \frac{70s - 268,125}{(s + 875 - j3000)} \right|_{s=-875-j3000} = \frac{70(-875 - j3000) - 268,125}{[(-875 - j3000) + 875 - j3000]} = 65.1 \angle -57.48^\circ$$

$$V_0(s) = \frac{65.1 \angle 57.48^\circ}{(s + 875 - j3000)} + \frac{65.1 \angle -57.48^\circ}{(s + 875 + j3000)}$$

$$v_0(t) = 2(65.1)e^{-875t} \cos(3000t + 57.48^\circ) = 130.2e^{-875t} \cos(3000t + 57.48^\circ)u(t) \text{ V}$$


Example 5

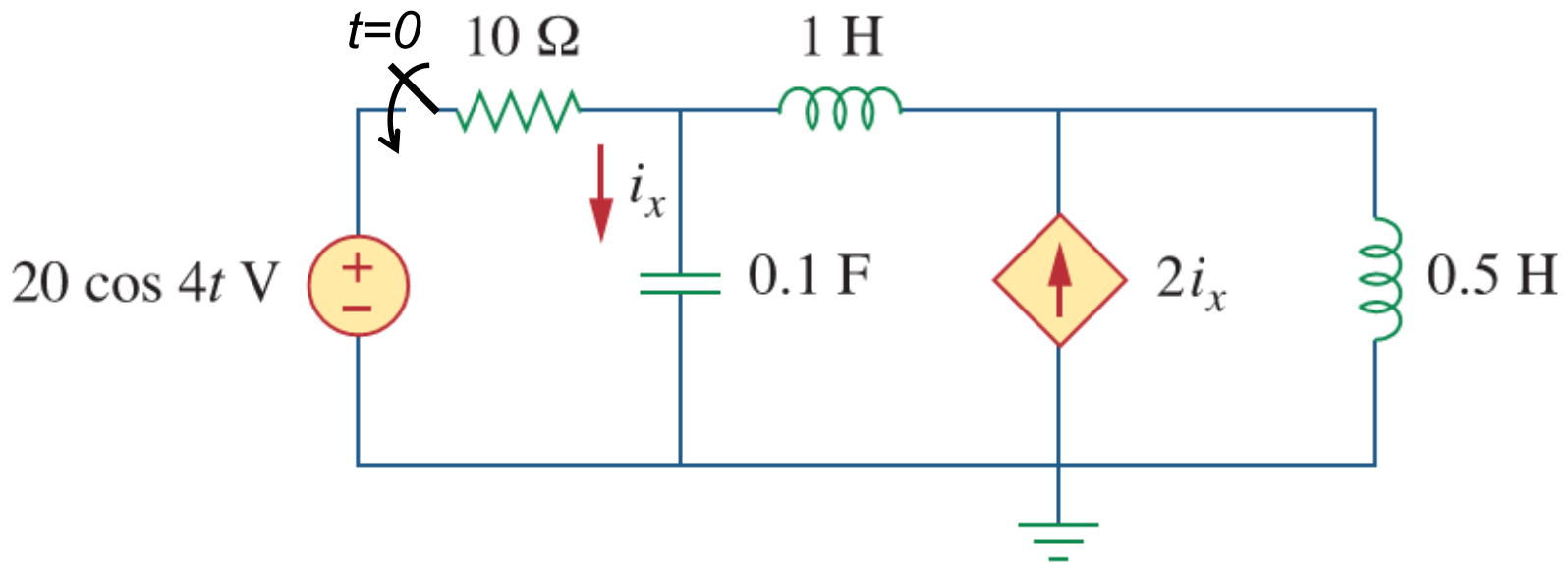- Example---Find i_x (s.s.) assuming no initial energy stored
Using phasor method and Laplace transform method






Phasor method

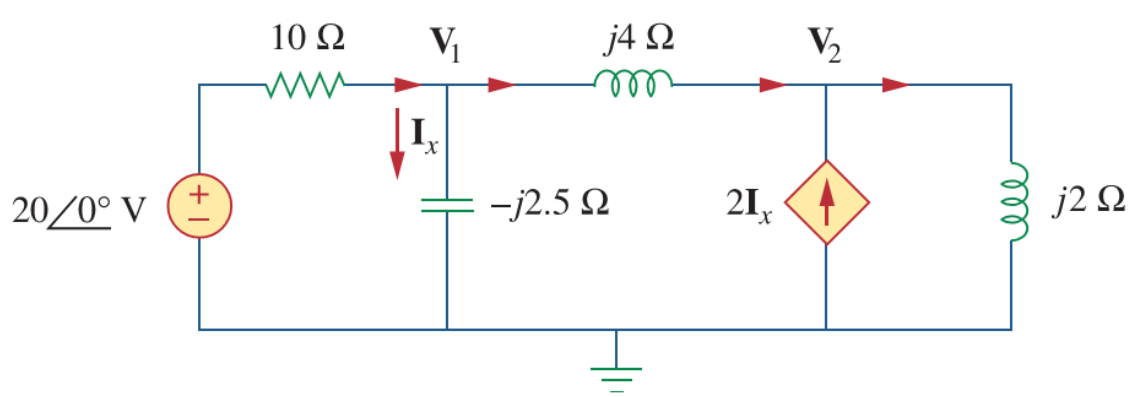
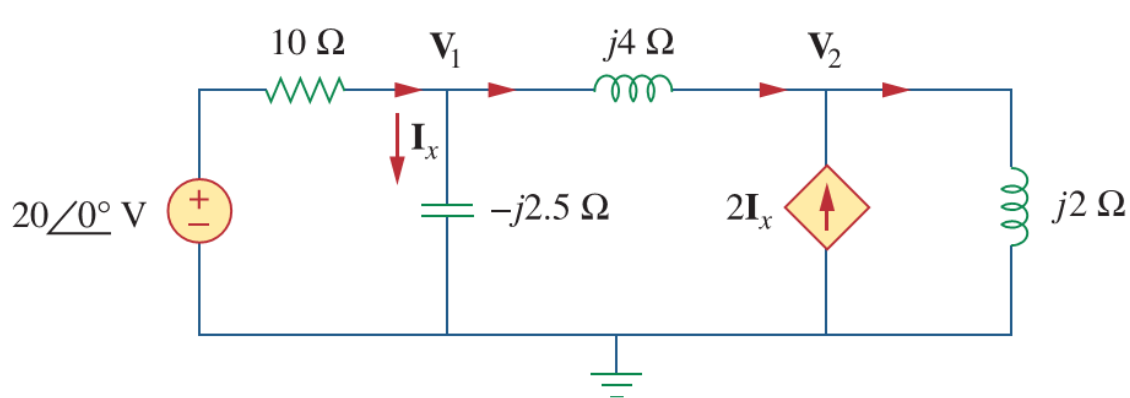
$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$



$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$
$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$



Laplace transform method to find i_x

